

University of Waterloo
Department of Mechanical and Mechatronics Engineering
ECE 140 – Linear Circuits
Final Examination – Winter 2025

SOLUTIONS

Date: April 9, 2025

Instructors: Section 1 – Derek Wright
 Section 2 – Mike Cooper-Stachowsky

- **Exam duration: 150 minutes**
- **Closed book, double-sided letter-sized crib sheet allowed**
- **Clearly indicate final answers**
- **Show your work for part marks**
- **Make and clearly state any necessary assumptions**
- **Scientific calculators allowed (graphing is permitted)**

Question	Marks
Q1	39
Q2	10
Q3	8
Q4	10
Q5	10
Q6	6
Total	83

Question 1 – Short Questions

39 Marks

Part a) [4 Marks]

Determine the voltages at nodes A and B, V_A and V_B .

$V_A = 20 \text{ V}$
$V_B = 12 \text{ V}$

KCL @ A:


$$5 = \frac{V_A}{5} + \frac{V_A - V_B}{8}$$

$$200 = 13V_A - 5V_B$$

KCL @ B:

$$\frac{V_B - V_A}{8} + \frac{V_B - 10}{2} = 0$$

$$5V_B - V_A = 40$$

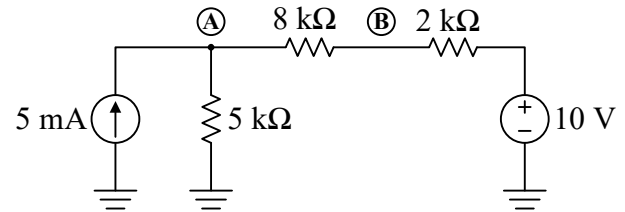

Solving:

$$200 = 13V_A - (40 + V_A)$$

$$240 = 12V_A$$

$$\therefore V_A = 20 \text{ V}$$

$$5V_B - 20 = 40$$

$$\therefore V_B = 12 \text{ V}$$


Part b) [3 Marks]

Determine V_{out} and I_{out} .

$V_{\text{out}} = 2.29 \text{ V}$
$I_{\text{out}} = 0 \text{ A}$

$I_{\text{out}} = 0 \text{ A}$ since output open-circuit.
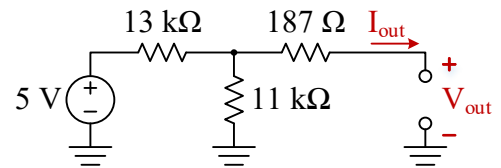
$$V_{\text{out}} = 5 \frac{11}{11 + 13} = 2.29 \text{ V}$$




No voltage drop across 187Ω resistor since $I_{\text{out}} = 0 \text{ A}$.

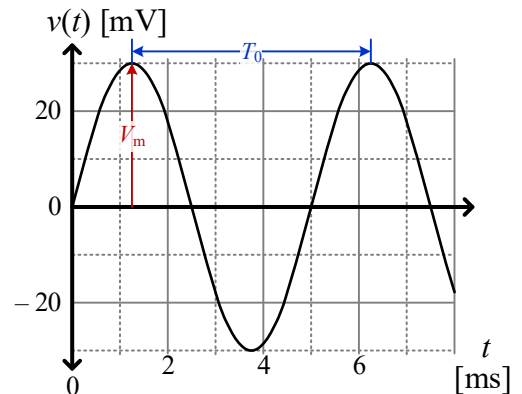Part c) [6 Marks]

Given the oscilloscope plot of $v(t)$, state the signal's peak voltage (the amplitude, $V_{\text{pk}} = V_m$), RMS voltage (V_{RMS}), period (T_0), and frequency in Hz (f_0) and rad/s (ω_0). Using the peak voltage (not RMS), write the phasor representation for this sinusoidal waveform, $\mathbf{V}$, in polar notation, including the correct units.


$V_m = 30 \text{ mV}_{\text{pk}}$
$V_{\text{RMS}} = V_m / \sqrt{2} = 21.2 \text{ mV}_{\text{RMS}}$
$T_0 = 5 \text{ ms}$
$f_0 = 1/T_0 = 200 \text{ Hz}$
$\omega_0 = 2\pi f_0 = 1.26 \text{ krad/s}$
$\mathbf{V} = 30 \angle -90^\circ \text{ mV}$



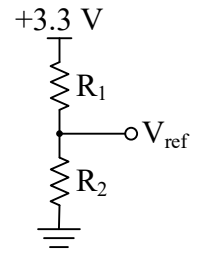Part d) [4 Marks]

Choose R_1 and R_2 so that $V_{\text{ref}} = 1.2 \text{ V}$ and the total power dissipated by R_1 and R_2 does not exceed 1 mW. Demonstrate through calculation that the power requirement is met.

$R_1 = 1.75R_2$ (6.93 k Ω min)
$R_2 = 3.96 \text{ k}\Omega$ min



Voltage constraint:

$$V_{\text{ref}} = 3.3 \frac{R_2}{R_1 + R_2}$$

$$1.2(R_1 + R_2) = 3.3R_2$$

$$R_1 = \frac{(3.3 - 1.2)R_2}{1.2} = \frac{2.1}{1.2}R_2 = 1.75R_2$$

Power constraint:

$$P_{\text{Total}} = P_{R_1} + P_{R_2} = \frac{V_{\text{Total}}^2}{R_{\text{Total}}} = \frac{3.3^2}{R_1 + R_2} \leq 1 \text{ mW}$$

$$\therefore \frac{3.3^2}{1 \text{ m}} \leq R_1 + R_2$$


$$R_1 + R_2 \geq 10.89 \text{ k}\Omega$$

At the lower limit, this leads to $R_1 = 6.93 \text{ k}\Omega$, and $R_2 = 3.96 \text{ k}\Omega$, so anything larger than these values that maintains the ratio is correct. It is also acceptable to choose a reasonable starting value and then demonstrate afterwards that the power requirement is met. For example, $R_2 = 10 \text{ k}\Omega$ gives $R_1 = 17.5 \text{ k}\Omega$, then show that $P_{\text{Total}} \leq 1 \text{ mW}$.

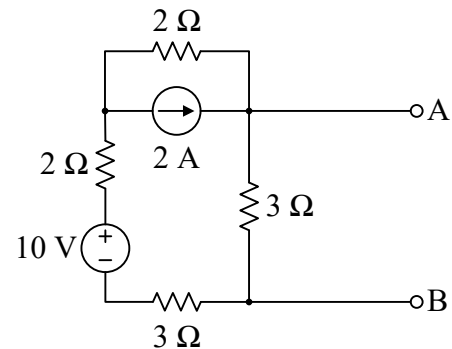
Part e) [3 Marks]

Determine the Thevenin equivalent circuit parameters, V_{Th} and R_{Th} , for node A with respect to node B.

$V_{\text{Th}} = 4.2 \text{ V}$
$R_{\text{Th}} = 2.1 \Omega$



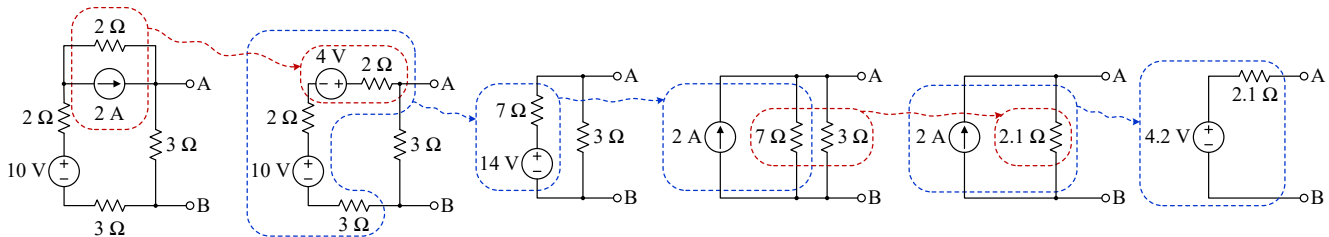Use whatever approach you're most comfortable with. Here is simplification via source transforms:



Part f) [4 marks]

Determine the resistance R_f , to achieve a closed-loop gain $A_{\text{ideal}} = 20 \text{ [V/V]}$. Assuming that **both resistors** have a $\pm 5\%$ tolerance, determine the worst-case maximum and minimum gains, A_{max} and A_{min} .


$R_f = 190 \text{ k}\Omega$
$A_{\text{max}} = 22 \text{ V/V}$
$A_{\text{min}} = 18.2 \text{ V/V}$

Noninverting amplifier:

$$A = 1 + \frac{R_f}{R_i}, \therefore R_f = (A - 1)R_i = (20 - 1) \times 10 \text{ k} = 190 \text{ k}\Omega$$

$$A_{\text{max}} = 1 + \frac{R_{f,\text{max}}}{R_{i,\text{min}}} = 1 + \frac{1.05 \times 190}{0.95 \times 10} = 22 \text{ V/V},$$

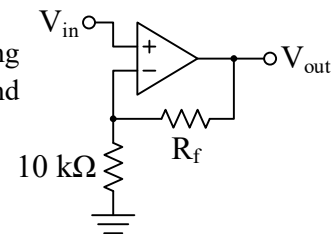
$$A_{\text{min}} = 1 + \frac{R_{f,\text{min}}}{R_{i,\text{max}}} = 1 + \frac{0.95 \times 190}{1.05 \times 10} = 18.2 \text{ V/V}.$$



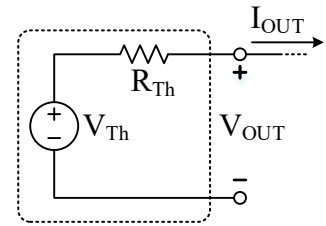Part g) [4 marks]

A lab voltage supply is modelled as a Thevenin-equivalent circuit, as shown. When two different loads are connected one after the other (not shown), the following two operating points are observed:

- $V_{OUT} = 3.298 \text{ V} @ I_{OUT} = 30 \text{ mA}$
- $V_{OUT} = 3.286 \text{ V} @ I_{OUT} = 270 \text{ mA}$



Determine the Thevenin-equivalent voltage and resistance of the output.

$V_{Th} =$	3.300 V	$R_{Th} = \frac{\Delta V_{OUT}}{\Delta I_{OUT}} = \frac{12 \text{ mV}}{240 \text{ mA}} = 50 \text{ m}\Omega$
$R_{Th} =$	50 mΩ	


If this wasn't apparent, you could use the KVL equation below with both data points to solve two equations in two unknowns. V_{Th} can be determined via KVL:

$$\begin{aligned}
 V_{Th} - I_{OUT}R_{Th} - V_{OUT} &= 0 \\
 V_{Th} - 30\text{m} \times 50\text{m} - 3.298 &= 0 \\
 \therefore V_{Th} &= 3.300 \text{ V}
 \end{aligned}$$

Part h) [6 Marks]

Determine the maximum and minimum allowable values of V_{in-} , $V_{in-,max}$ and $V_{in-,min}$.

$V_{in-,max} =$	2.25 V	This is a difference amplifier: $V_{out} = \frac{R_f}{R_i} (V_{in+} - V_{in-}) = \frac{47}{4.7} (2 - V_{in-})$ $= 20 - 10V_{in-}$
$V_{in-,min} =$	1.5 V	

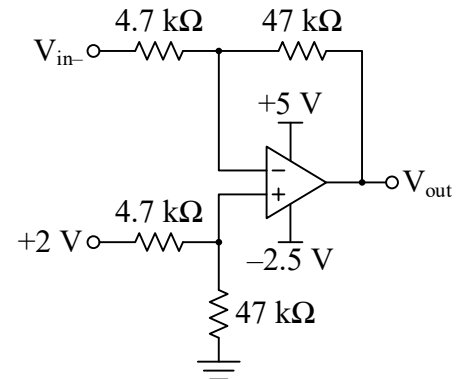

When V_{in-} increases, V_{out} decreases, and vice versa. So, $V_{in-,max}$ will be associated with the *minimum* allowable output voltage (-2.5 V) and $V_{in-,min}$ will be associated with the maximum allowable output voltage ($+5 \text{ V}$):

$$V_{out,min} = -2.5 = 20 - 10V_{in-,max} \therefore V_{in-,max} = 2.25 \text{ V}$$

$$V_{out,max} = 5 = 20 - 10V_{in-,min} \therefore V_{in-,min} = 1.5 \text{ V}$$

Part i) [5 Marks]

Lab Safety: Circle the most correct answer for each question.

1) What type of footwear is not allowed in the lab?

- A. Sneakers
- B. Running shoes
- C. Sandals**
- D. Boots

2) Why is it dangerous to bring liquids into the lab?

- A. They can cause fire or electrocution.**
- B. They could stain the lab manuals.
- C. They can damage the breadboards.
- D. It's just a general rule.

3) When preparing to measure current using a multimeter, which configuration is safe and correct?

- A. Connect the meter in parallel with the powered circuit and set it to voltage mode.
- B. Connect the meter directly across any charged capacitors and set it to resistance mode.
- C. Connect the meter in parallel with the circuit component and set it to current mode.
- D. Connect the meter in series with the powered circuit and set it to current mode.**

4) You notice a frayed power cable on your lab power supply. What should you do?

- A. Wrap the frayed cable securely with electrical tape and continue using it.
- B. Inform your lab instructor immediately and avoid using the equipment.**
- C. Switch the unit off periodically to prevent overheating.
- D. Handle the cable carefully, avoiding direct contact with the frayed area.

5) Before changing components in your circuit, you must first:

- A. Lower the voltage slightly to avoid large current spikes.
- B. Turn off the power supply and discharge all capacitors.**
- C. Ground the negative terminal of your power supply to the lab bench.
- D. Confirm the circuit is functioning correctly to avoid misdiagnosing faults.

Question 2

[10 Marks]

Find the unknown node voltages and circle the supernode.


$V_A = 20 \text{ V}$
$V_B = 14 \text{ V}$
$V_C = 4 \text{ V}$

$$1.5V_C = \frac{V_A}{10} + \frac{V_A - V_B}{1.5}$$

$$\frac{V_B - V_A}{1.5} + \frac{V_C}{2} + \frac{V_B}{7} = 0$$

$$V_B = V_C + 10$$

Supernode in red

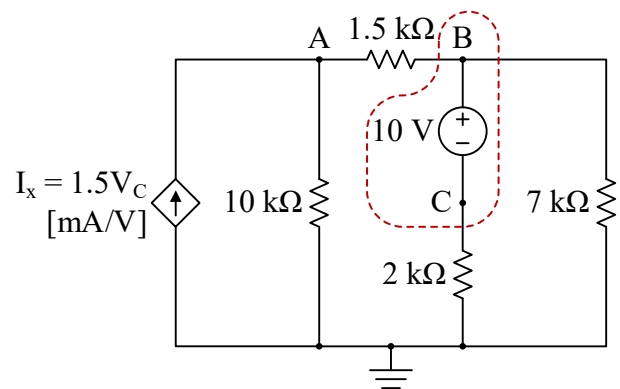

Question 3

[8 Marks]

Determine V_A , V_{out} , I_1 , and I_2 .

$V_A = -0.4 \text{ V}$
$V_{out} = -6.8 \text{ V}$
$I_1 = 20 \mu\text{A}$
$I_2 = 112 \mu\text{A}$

It's almost an inverting amplifier, but the feedback network looks too complicated to use $A = -R_f/R_i$. Since there's CLNF, start there. The opamp sets $V_- = V_+ = 0 \text{ V}$. We can now do nodal at V_- and V_A :

KCL @ V_- :

$$\frac{V_- - 0.12}{6} + \frac{V_- - V_A}{20} = 0$$

Since $V_- = 0 \text{ V}$:

$$-\frac{0.12}{6} - \frac{V_A}{20} = 0$$

$$\therefore V_A = -0.4 \text{ V}$$


KCL @ V_A :

$$\frac{V_A - V_-}{20} + \frac{V_A - 0}{60} + \frac{V_A - V_{out}}{240} = 0$$

$$\frac{0.4}{20} + \frac{0.4}{60} + \frac{0.4 + V_{out}}{240} = 0$$

$$\therefore V_{out} = -6.8 \text{ V}$$
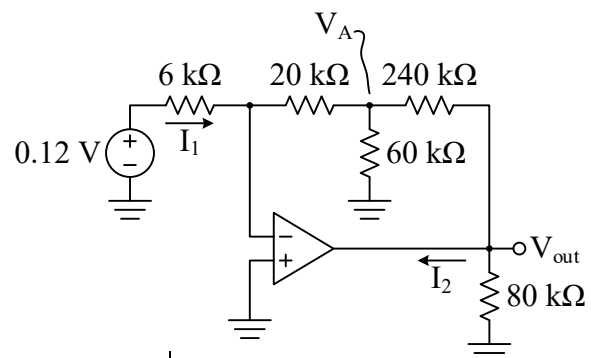
$$I_1 = \frac{0.12 - 0}{6} = 20 \mu\text{A}$$



KCL @ V_{out} to get I_2 :

$$\frac{V_{out} - V_A}{240} + \frac{V_{out}}{80} + I_2 = 0$$

$$\frac{-6.8 - (-0.4)}{240} + \frac{-6.8}{80} + I_2 = 0$$


$$\therefore I_2 = 112 \mu\text{A}$$

Question 4

[10 Marks]

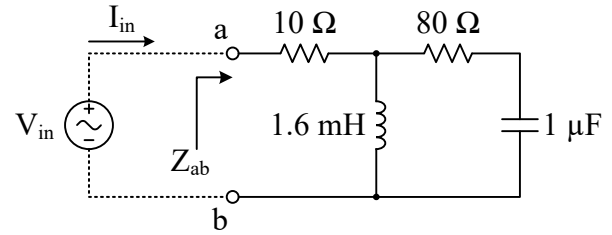Part a) [5 Marks]

Given $\omega_0 = 25 \text{ krad/s}$, determine the impedances of L and C (Z_L , and Z_C , respectively), and the equivalent impedance at node a with respect to node b, Z_{ab} .



$Z_L =$	$j40 \Omega = 40\angle 90^\circ \Omega$
$Z_C =$	$-j40 \Omega = 40\angle -90^\circ \Omega$
$Z_{ab} =$	$30 + j40 \Omega = 50\angle 53^\circ \Omega$

$$Z_L = j\omega_0 L = j \times 25\text{k} \times 1.6\text{m} = j40 \Omega = 40\angle 90^\circ \Omega$$

$$Z_C = \frac{1}{j\omega_0 C} = -\frac{j}{25\text{k} \times 1\mu} = -j40 \Omega = 40\angle -90^\circ \Omega$$

$$\begin{aligned} Z_{ab} &= 10 + [Z_L \parallel (80 + Z_C)] \\ &= 10 + [j40 \parallel (80 - j40)] \\ &= 10 + \left(\frac{1}{j40} + \frac{1}{80 - j40} \right)^{-1} \\ &= 10 + \left(\frac{80 - j40 + j40}{j40(80 - j40)} \right)^{-1} \\ &= 10 + \frac{j40(80 - j40)}{80} \\ &= 10 + j20(2 - j) \\ &= 10 + j40 + 20 \\ &= 30 + j40 \Omega = 50\angle 53^\circ \Omega \end{aligned}$$

Part b) [2 Marks]

The voltage applied to node a is $V_{in} = 10\angle 0^\circ V_{\text{RMS}}$. Determine the current entering the circuit, I_{in} .

$I_{in} =$	$0.12 - j0.16 \text{ A} = 0.2\angle -53^\circ \text{ A}$
------------	--

$$I_{in} = \frac{V_{in}}{Z_{ab}} = \frac{10\angle 0^\circ}{50\angle 53^\circ} = 0.12 - j0.16 \text{ A} = 0.2\angle -53^\circ \text{ A}$$

Part c) [3 Marks]

Determine the real and reactive power at the input, P_{in} and Q_{in} , respectively. Then, express this as a complex power phasor, S_{in} . Be sure to include the correct units.


$P_{in} =$	1.2 W
$Q_{in} =$	1.6 VAR
$S_{in} =$	$1.2 + j1.6 \text{ VA} = 2\angle 53^\circ \text{ VA}$

$$S_i = V_{in} I_{in}^* = 10(0.12 + j0.16) = 1.2 + j1.6 \text{ VA} = 2\angle 53^\circ \text{ VA}$$

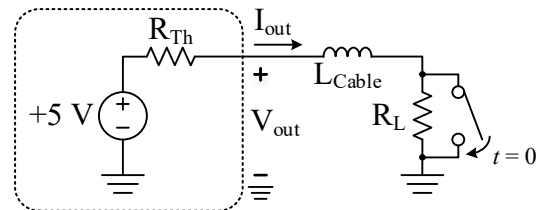Question 5

[10 Marks]

The Thevenin equivalent circuit of a 5 V USB charger output is shown in the dashed box of Figure a). A long cable with inductance L_{Cable} connects the charger output to a load, R_L .



Part a) [4 Marks]

$R_{Th} =$	50 Ω
$I_{out} =$	497.5 μA

Ignore the switch for now. When no load is connected, $V_{out} = 5.000$ V. However, V_{out} stabilizes at 4.975 V when a load $R_L = 10$ k Ω is connected. Determine R_{Th} and I_{out} .

$$V_{out} = V_{Th} \frac{R_L}{R_L + R_{Th}}, \therefore R_{Th} = \frac{V_{Th} R_L}{V_{out}} - R_L = \frac{5 \times 10k}{4.975} - 10k = 50 \Omega$$

$$I_{out} = \frac{V_{out}}{R_L} = \frac{4.975}{10k} = 497.5 \mu A$$

Part b) [6 Marks]

L_{Cable} is measured to be 4 μH . A short occurs at time $t = 0$, modelled as a switch closing around R_L . Determine an expression for the output current, $I_{out}(t)$, valid for $t \geq 0$. Determine $V_{out}(t = 100$ ns)

$I_{out}(t) =$	100 – 99.5$e^{-\frac{t}{80n}}$ [mA]
$V_{out}(t = 100$ ns) =	1.425 V

$$I_i = 497.5 \mu A$$

$$I_f = I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{5}{50} = 100 \text{ mA}$$

$$\tau = \frac{L_{Cable}}{R_{Th}} = \frac{4\mu}{50} = 80 \text{ ns}$$

$$\therefore I_{out}(t) = I_f + (I_i - I_f)e^{-\frac{t}{\tau}} = 100 - 99.5e^{-\frac{t}{80n}} \text{ [mA]}$$

Given this current, the output voltage is determined by the drop across R_{Th} :


$$I_{out}(t = 100 \text{ ns}) = 100 - 99.5e^{-\frac{100n}{80n}} \text{ [mA]} = 71.5 \text{ mA}$$

$$V_{out}(t = 100 \text{ ns}) = V_{Th} - I_{out}(t = 100 \text{ ns})R_{Th} = 5 - 71.5m \times 50 = 1.425 \text{ V}$$

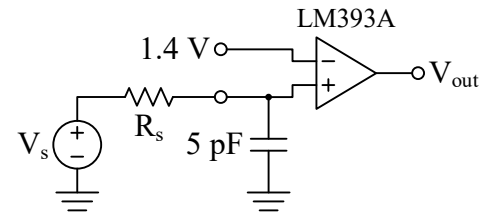Question 6

[6 Marks]

A sensor generates a step output voltage signal, $V_s = 0 \rightarrow 5$ V when a dangerous material falls during handling. The system must be immediately disabled when V_s exceeds 1.4 V **with no more than a 3 μs delay**. An opamp comparator (LM393A) ensures there is minimal output delay once $V_+ > V_-$, however, the sensor's output resistance, R_s , interacts with the comparator's 5 pF input capacitance to cause an RC switching delay.



Assuming that the sensor triggers ($V_s = 0 \rightarrow 5$ V) at $t = 0$, determine the maximum allowable sensor output resistance, $R_{s,max}$, so that the noninverting input voltage $V_+ = 1.4$ V at $t = 3 \mu s$. Anything larger than this resistance causes a time constant that is too slow.

$$V_i = 0 \text{ V}, V_f = 5 \text{ V}, \tau = R_s C_+$$

$$V_+(t) = V_f + (V_i - V_f)e^{-\frac{t}{R_s C_+}} = 5 - 5e^{-\frac{t}{R_s 5p}}$$

$$\therefore 1.4 = 5 - 5e^{-\frac{3\mu}{R_{s,max} \times 5p}}$$

$$e^{-\frac{600k}{R_{s,max}}} = 0.72, \therefore R_{s,max} = -\frac{600k}{\ln 0.72} = 1.83 \text{ M}\Omega$$